

Resistance

- Resistance is what causes the load to convert electrical energy into heat energy
- Resistances are the barriers to the flow of charge
 - Resistance is calculated using Ohms Law

$$R = V/I$$

- The Unit of resistance is ohms Ω

Factors that Affect Resistance


- Length of Wire
 - Eg. Extension cords heating up
 - Longer the wires the more resistance
- Cross Sectional Area
 - Larger the cross sectional area the less the resistance
- Temperature
 - Higher the temperature the more the resistance
 - The longer devices are used, the warmer wires get and the less efficient they become.
- Material
 - Some materials are better conductors than others
 - E.g. copper is a better conductor than iron

There are 3 variations of the formula

- o $V = I * R$

- o $I = V/R$

- o $R = V/I$

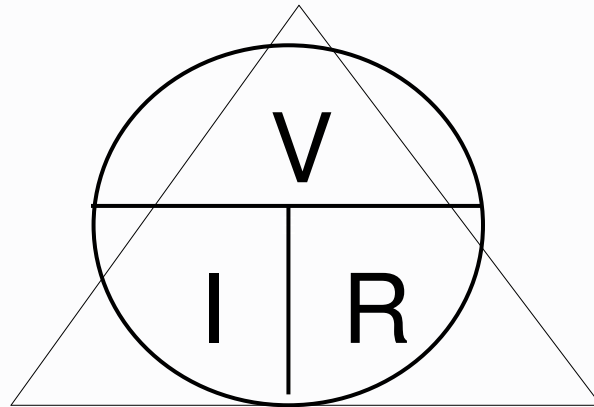

Using the GRASS PROBLEM SOLVING METHOD

- o GIVEN

- o REQUIRED

- o ANALYSIS

- o SOLUTION

- o STATEMENT

Calculate the Resistance Using Ohms Law


What is the resistance of the resistor in the following circuit?

Given

$$I = 4 \text{ A}$$

$$V = 12 \text{ V}$$

$$R = ? \Omega$$

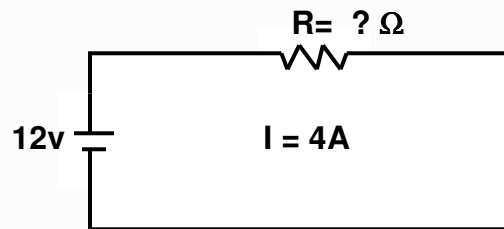

Calculate Current Using Ohms Law

A 4v battery is placed in a series circuit with a 2Ω resistor.


What is the total current that will flow through the circuit?

Given

$$R = 2 \Omega$$

$$V = 4 \text{ V}$$

$$I = ?$$

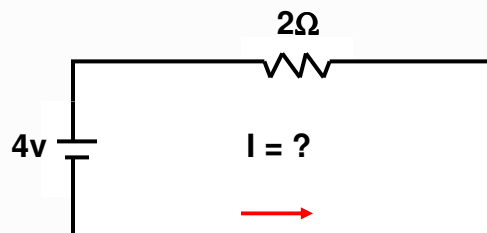

Calculate the Voltage using Ohms Law


What voltage is required to produce 2a though a circuit with a 3Ω resistor.

Given

$$I = 2 \text{ A}$$

$$R = 3\Omega$$

$$V = ?$$

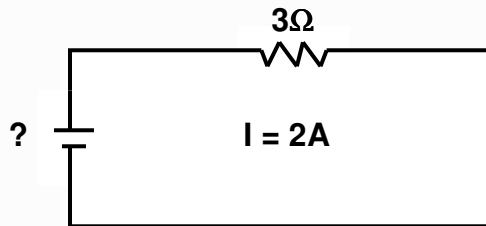

More Complex Problem Solving

Problem Solving


Resistance in series sum together when calculating total resistance

What is the current in the circuit below?

$$V = 12\text{ V}$$

$$R_{\text{total}} = 2\Omega + 4\Omega$$

$$I = ?$$

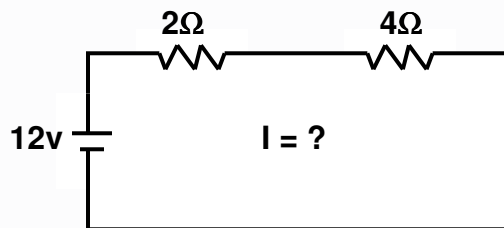

Problem Solving

What is the voltage of the resistor?

What is the Voltage of the light bulb?

$$V = IR$$

